

# Contents

<b>Chapter 1: Hall-Effect Physics .....</b>	<b>1</b>
1.1 A Quantitative Examination.....	3
1.2 Hall Effect in Metals.....	5
1.3 The Hall Effect in Semiconductors.....	7
1.4 A Silicon Hall-Effect Transducer.....	9
<b>Chapter 2: Practical Transducers.....</b>	<b>11</b>
2.1 Key Transducer Characteristics .....	11
Sensitivity.....	11
Temperature Coefficient of Sensitivity .....	12
Ohmic Offset.....	13
Temperature Coefficient of Ohmic Offset .....	14
Linearity.....	14
Input and Output Resistances.....	14
Temperature Coefficient of Resistance .....	15
Noise .....	15
2.2 Bulk Transducers .....	16
2.3 Thin-Film Transducers.....	17
2.4 Integrated Hall Transducers .....	20
2.5 Transducer Geometry.....	26
2.6 The Quad Cell.....	27
2.7 Variations on the Basic Hall-Effect Transducer.....	30
2.8 Examples of Hall Effect Transducers.....	33

<b>Chapter 3: Transducer Interfacing .....</b>	<b>35</b>
3.1 An Electrical Transducer Model .....	36
3.2 A Model for Computer Simulation .....	38
3.3 Voltage-Mode Biasing.....	41
3.4 Current-Mode Biasing .....	45
3.5 Amplifiers .....	48
3.6 Amplifier Circuits .....	51
3.7 Analog Temperature Compensation.....	54
3.8 Offset Adjustment .....	57
3.9 Dynamic Offset Cancellation Technique .....	58
<b>Chapter 4: Integrated Sensors: Linear and Digital Devices .....</b>	<b>61</b>
4.1 Linear Sensors.....	62
4.2 Linear Transfer Curve .....	65
4.3 Drift.....	66
4.4 Ratiometry.....	67
4.5 Output Characteristics.....	68
4.6 Bandwidth .....	69
4.7 Noise .....	71
4.8 Power Supply Requirements for Linear Sensors .....	71
4.9 Temperature Range .....	72
4.10 Field-Programmable Linear Sensors.....	72
4.11 Typical Linear Devices .....	74
4.12 Switches and Latches .....	75
4.13 Definition of Switch vs. Latch .....	77
4.14 Switchpoint Stability.....	78
4.15 Bipolar Switches .....	78
4.16 Power Supply Requirements for Digital Sensors.....	79
4.17 Output Drivers.....	80
4.18 Typical Digital Devices.....	81
<b>Chapter 5: Interfacing to Integrated Hall-Effect Devices.....</b>	<b>83</b>
5.1 Interface Issues—Linear Output Sensors .....	83
5.2 Offset and Gain Adjustment.....	84

5.3	Output Thresholding .....	86
5.4	Interfacing to Switches and Latches .....	88
5.5	The Pull-Up Resistor.....	88
5.6	Interfacing to Standard Logic Devices .....	90
5.7	Discrete Logic .....	91
	Logic NOT Output .....	92
	Wired OR Output.....	93
	AND function.....	93
5.8	Driving Loads .....	93
5.9	LED Interfaces.....	93
5.10	Incandescent Lamps.....	94
5.11	Relays, Solenoids, and Inductive Loads .....	96
5.12	Wiring-Reduction Schemes .....	98
5.13	Encoding and Serialization .....	98
5.14	Digital-to-Analog Encoding.....	99
5.15	Mini-Networks.....	102
5.16	Voltage Regulation and Power Management .....	104

## **Chapter 6: Proximity-Sensing Techniques ..... 107**

6.1	Head-On Sensing .....	107
6.2	Slide-By Sensing.....	109
6.3	Magnet Null-Point Sensing.....	110
6.4	Float-Level Sensing .....	114
6.5	Linear Position Sensing .....	116
6.6	Rotary Position Sensing.....	118
6.7	Vane Switches .....	122
6.8	Some Thoughts on Designing Proximity Sensors .....	126

## **Chapter 7: Current-Sensing Techniques..... 131**

7.1	Resistive Current Sensing .....	131
7.2	Free-Space Current Sensing.....	133
7.3	Free-Space Current Sensors II .....	136
7.4	Toroidal Current Sensors .....	140
7.5	Analysis of Slotted Toroid .....	142

7.6	Toroid Material Selection and Issues .....	143
7.7	Increasing Sensitivity with Multiple Turns .....	144
7.8	An Example Current Sensor .....	145
7.9	A Digital Current Sensor .....	146
7.10	Integrated Current Sensors.....	147
7.11	Closed-Loop Current Sensors.....	148
<b>Chapter 8: Speed and Timing Sensors.....</b>		<b>151</b>
8.1	Competitive Technologies.....	151
8.2	Magnetic Targets .....	153
8.3	Vane Switches .....	155
8.4	Geartooth Sensing.....	157
8.5	Geartooth Sensor Architecture.....	158
8.6	Single-Point Sensing .....	159
8.7	Single-Point/Fixed-Threshold Schemes.....	161
8.8	Single-Point/Dynamic-Threshold Schemes.....	163
8.9	Differential Geartooth Sensors.....	167
8.10	Differential Fixed-Threshold .....	169
8.11	Differential Variable-Threshold .....	170
8.12	Comparison of Hall-Effect Speed Sensing Methods .....	171
8.13	Speed and Direction Sensing .....	171
8.14	How Fast Do Speed Sensors Go? .....	173
<b>Chapter 9: Application-Specific Sensors.....</b>		<b>177</b>
9.1	Micropower Switches .....	177
9.2	Two-Wire Switches .....	180
9.3	Power Devices.....	182
9.4	Power + Brains = Smart Motor Control.....	183
<b>Chapter 10: Development Tools.....</b>		<b>187</b>
10.1	Electronic Bench Equipment .....	187
	Power supplies .....	187
	Voltmeters and DMMs .....	188
	Oscilloscope.....	189
	Frequency Counter.....	189

Clamp-On Current Probes .....	189
Solderless Breadboard .....	190
10.2 Magnetic Instrumentation .....	190
Gaussmeter .....	190
Fluxmeter .....	191
Calibrated Hall-Effect ICs .....	192
Polarity probe .....	192
Magnetic View Film .....	193
Magnetizers and Magnet Conditioners .....	193
Helmholtz Coil .....	195
10.3 Mechanical Tools .....	196
Optical Bench .....	196
Linear Positioning Slides .....	196
Rotary Table .....	197
Calipers and Micrometers .....	197
Machine Tools .....	198
Environmental Chamber .....	199
10.4 Magnetic Simulation Software .....	199
<b>Appendix A: A Brief Introduction .....</b>	<b>203</b>
A.1 Where Magnetic Fields Come From .....	203
A.2 Magnetic Materials .....	205
A.3 Some Permanent Magnet Materials .....	210
<b>Appendix B: Supplier List .....</b>	<b>211</b>
<b>Appendix C: Glossary of Common Terms .....</b>	<b>219</b>
<b>Appendix D: References and Bibliography .....</b>	<b>229</b>
<b>About the Author .....</b>	<b>231</b>
<b>Index .....</b>	<b>233</b>